

INDRAPRASTHA INSTITUTE OF INFORMATION TECHNOLOGY, DELHI
ECE111 DC


TUTORIAL 3

(Answer any 9 out of 12 Questions, 7th Question is a compulsory Question)

Total Marks: 10

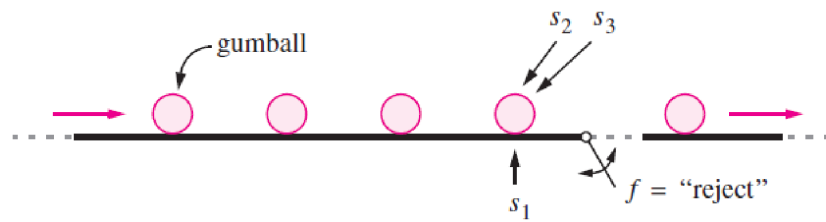1. Convert the following decimal numbers into binary (1 marks)
 - a. $(17)_{10}$
 - b. $(33)_{10}$
 - c. $(130)_{10}$
 - d. $(2560)_{10}$
2. What is the minimum number of bits needed to represent the following decimal numbers in binary? (1 marks)
 - a. $(270)_{10}$
 - b. $(520)_{10}$
 - c. $(780)_{10}$
 - d. $(1029)_{10}$
3. Prove the validity of the logic equation (1 marks)
 - i. $(x_1 + x_3) \cdot (\overline{x_1} + \overline{x_3}) = \overline{x_1} \cdot \overline{x_3} + x_1 \cdot x_3$
 - ii. $x_1 \cdot \overline{x_3} + x_1 \cdot x_3 + \overline{x_2} \cdot \overline{x_3} + \overline{x_2} \cdot x_3 = x_1 + \overline{x_2}$
4. Implement the following logic function: (1 marks)
 - i. $F(x_1, x_2) = x_1 \cdot x_2 + \overline{x_1} \cdot \overline{x_2} + \overline{x_1} \cdot x_2$
 - ii. $F(s_1, s_2, s_3) = \overline{s_1} \cdot \overline{s_2} \cdot s_3 + \overline{s_1} \cdot s_2 \cdot s_3 + s_1 \cdot \overline{s_2} \cdot s_3 + s_1 \cdot s_2 \cdot \overline{s_3} + s_1 \cdot s_2 \cdot s_3$
5. Use algebraic manipulation to prove following: (1 marks)
 - i. $(x + y) \cdot (x + y) = x + y$
 - ii. $x \cdot y + y \cdot z + x \cdot z = x \cdot y + x \cdot z$
6. Determine whether or not the following expressions are valid, i.e., whether the left- and right-hand sides represent the same function. (1 marks)
 - (a) $\overline{x_1}x_3 + x_1x_2\overline{x_3} + \overline{x_1}x_2 + x_1\overline{x_2} = \overline{x_2}x_3 + x_1\overline{x_3} + x_2\overline{x_3} + \overline{x_1}x_2x_3$
 - (b) $x_1\overline{x_3} + x_2x_3 + \overline{x_2}\overline{x_3} = (x_1 + \overline{x_2} + x_3)(x_1 + x_2 + \overline{x_3})(\overline{x_1} + x_2 + \overline{x_3})$
 - (c) $(x_1 + x_3)(\overline{x_1} + \overline{x_2} + \overline{x_3})(\overline{x_1} + x_2) = (x_1 + x_2)(x_2 + x_3)(\overline{x_1} + \overline{x_3})$
7. Figure 1 depicts a part of a factory that makes bubble gumballs. The gumballs travel on a conveyor that has three associated sensors s_1 , s_2 , and s_3 . The sensor s_1 is connected to a scale that weighs each gumball, and if a gumball is not heavy enough to be acceptable then the sensor sets $s_1 = 1$. Sensors s_2 and s_3 examine the diameter of each gumball. If a gumball is too small to be acceptable, then $s_2 = 1$, and if it is too large, then $s_3 = 1$. If a gumball is of an acceptable weight and size, then the sensors give $s_1 = s_2 = s_3 = 0$. The conveyor pushes the gumballs over a “trap door” that it used to reject the ones that are not properly formed. A gumball should be rejected if it is too large, or both too small and too

light. The trap door is opened by setting the logic function f to the value 1. By inspection, we can see that an appropriate logic expression is $f = s_1s_2 + s_3$. Use Boolean algebra to derive this logic expression from the truth table and implement the logic function using AND, OR and NOT gate. (2 marks)



(a) Conveyor and sensors

Figure 1

8. Design the simplest sum-of-products circuit that implements the function (1 marks)

i. $f(x, y, z) = \sum m(3, 4, 6, 7)$

ii. $f(x, y, z) = \sum m(1, 3, 4, 6, 7)$

9. Design the simplest product-of-sums circuit that implements the function (1 marks)

i. $f(x, y, z) = \prod M(0, 2, 5).$

ii. $f(x, y, z) = \prod M(0, 1, 5, 7)$

10. Derive the simplest sum-of-products expression for the function (1 marks)

$$f(w, x, y, z) = w \cdot \bar{y} \cdot \bar{z} + x \cdot \bar{y} \cdot z + w \cdot x \cdot y$$

11. Derive the simplest product-of-sums expression for the function (1 marks)

$$f(w, x, y, z) = (w + y + z) \cdot (x + y + z) \cdot (w + x + y)$$

12. Design the simplest circuit that has three inputs, x_1 , x_2 , and x_3 , which produces an output value of 1 whenever two or more of the input variables have the value 1; otherwise, the output must be 0. (1 marks)