

QUIZ 3

ECE 111 DIGITAL CIRCUITS

Date: March 14, 2022.


Time: 8:00 – 8:20 PM.

Max. Marks: 10


ANSWER ALL QUESTIONS

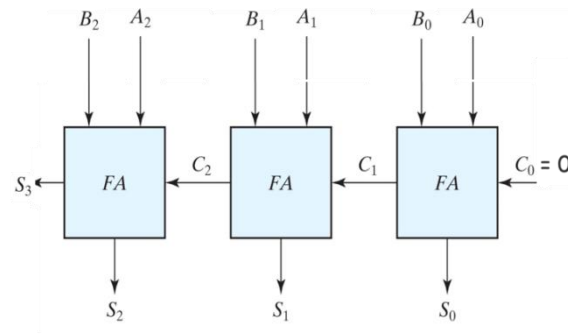1. A 3-bit offset binary code is given by the equivalence: $-4 = 000$, $-3 = 001$, $-2 = 010$, $-1 = 011$, $0 = 100$, $+1 = 101$, $+2 = 110$, $+3 = 111$. This scheme is used in Analog to Digital and Digital to Analog conversions. Give an approach to design an adder that adds two 3-bit offset-binary numbers and gives the 4-bit result in the 4-bit offset-binary format.

Use a three-bit full adder two 3-bit offset-binary numbers. The three sum bits along with the final carry bit gives the 4-bit offset-binary number.



or

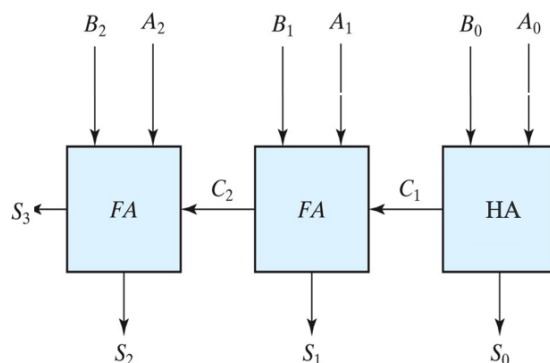

The students can use three FAs with $C_0 = 0$ or two FAs and one HA. The final carry out is the MSB of the result.