

QUIZ 2

ECE 111 DIGITAL CIRCUITS

Date: March 7, 2022.

Max. Marks: 10

ANSWER ALL QUESTIONS

- Figure 1 shows the symbol of 74154 4 to 16 decoder. Using this decoder, give the logic circuit realization for the following logic functions using 74154 and minimum number of logic gates.

$$f_1(W, X, Y, Z) = \sum m(1, 9, 12, 15)$$

$$f_2(W, X, Y, Z) = \sum m(0, 1, 2, 3, 4, 5, 7, 8, 10, 11, 12, 13, 14, 15)$$

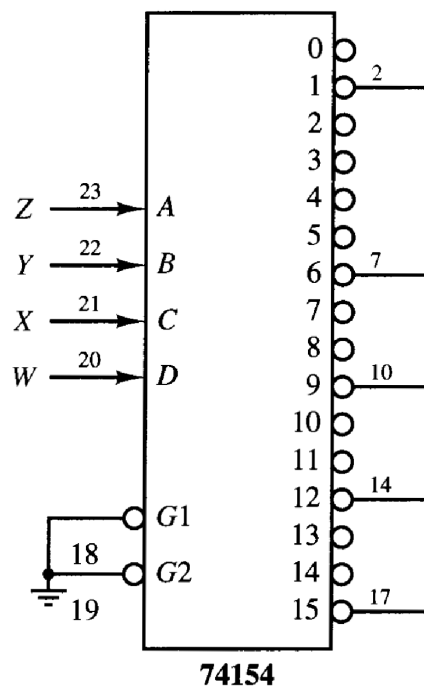


Figure 1

ANS:

We have  $f_1 = A'B'C'D + A'B'CD' + A'BC'D' + AB'C'D' = \overline{m_1} + \overline{m_9} + \overline{m_{12}} + \overline{m_{15}}$  and **1.5**

**marks**


$$f_2 = \overline{m_6} + \overline{m_9}$$

**1.5**

**marks**

For any other minimised expression one mark each.

The realisation is shown below:

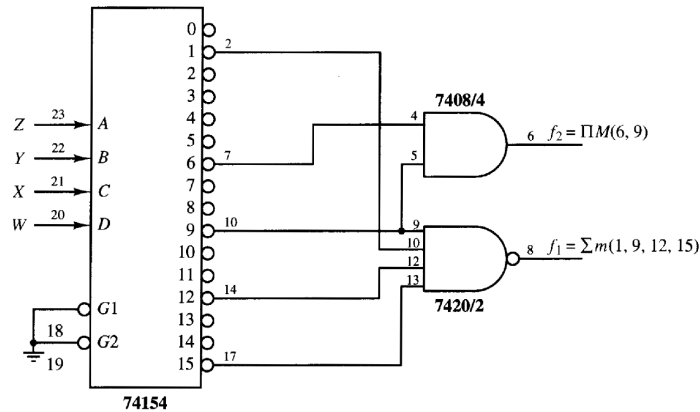


2 Marks

2. Realise logic function  $F = \sum (2, 3, 6, 7, 12, 13, 14, 15, 18, 19, 21, 23, 26, 27, 29, 31)$  using minimum number of two inputs 2:1 MUX.

ANS:


Karnaugh Map:

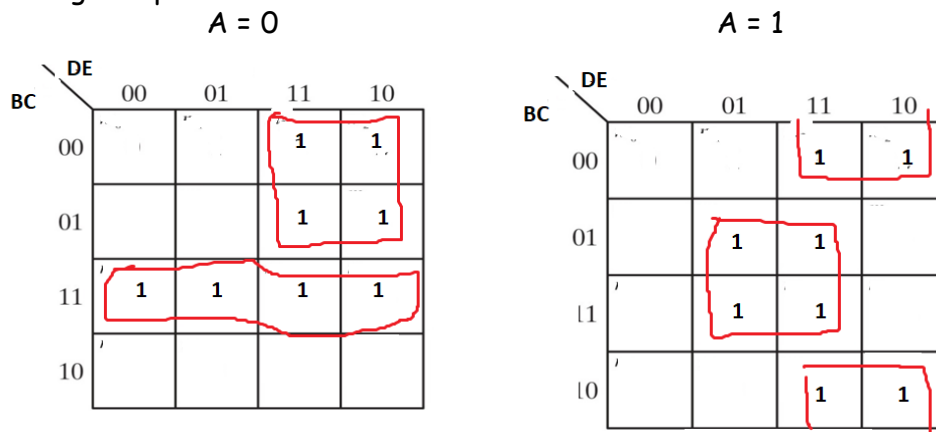

2 Mark

$F = A [CE + C' D] + A' [BC + B' D]$  By using Karnaugh map. The realization is shown below.

1Mark

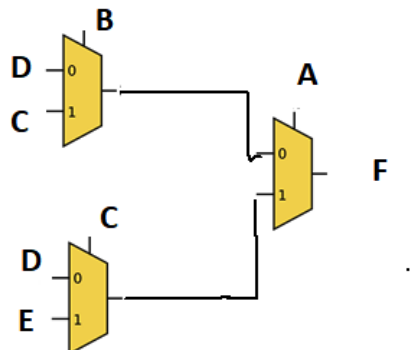

2 Marks