

Q1.

Ans 1:

	S_4	S_3	S_2	S_1	R	G
0	0	0	0	0	X	X
1	0	0	0	1	0	0
2	0	0	1	0	0	1
3	0	0	1	1	0	1
4	0	1	0	0	1	0
5	0	1	0	1	X	X
6	0	1	1	0	1	0
7	0	1	1	1	1	0
8	1	0	0	0	1	1
9	1	0	0	1	X	X
10	1	0	1	0	X	X
11	1	0	1	1	X	X
12	1	1	0	0	1	1
13	1	1	0	1	X	X
14	1	1	1	0	1	1
15	1	1	1	1	1	1

X \rightarrow Don't Care Cond'n

(S_2 : priority)

(S_3 : priority)

(S_4 : priority)

(S_4 : priority)

$S_4 S_3 \backslash S_2 S_1$

	00	01	11	10
00	X ₀		1	3
01	1 ₄	X ₅	1 ₇	1 ₆
11	1 ₁₂	X ₁₃	1 ₁₅	1 ₁₄
10	1 ₈	X ₉	X ₁₁	X ₁₀

$S_4 S_3 \backslash S_2 S_1$

	00	01	11	10
00	X ₀		1 ₃	1 ₂
01	0 ₄	X ₅	7	6
11	1 ₁₂	X ₁₃	1 ₁₅	1 ₁₄
10	1 ₈	X ₉	X ₁₁	X ₁₀

$R \Rightarrow S_3 + S_4$ Ans

$G = S_4 + \bar{S}_3 S_2$ Ans

Combinational circuit:

```


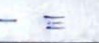
graph LR
    S3 --> OR1
    S4 --> OR1
    OR1 --> R
    S4 --> AND1
    S2 --> AND1
    NOT_S3[NOT S3] --> AND1
    AND1 --> OR2
    OR2 --> G
  
```


Ans


Q2.

Ans 2 : Driver reaches on time $A=1$
 Total number of passengers are equal or greater than 10
 $\rightarrow B=1$
 No rain $C=1$

$P = ABC$ (traveling at 60kmph)
 $P = \overline{ABC}$

*  \equiv 

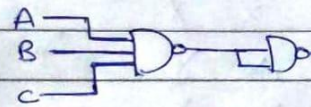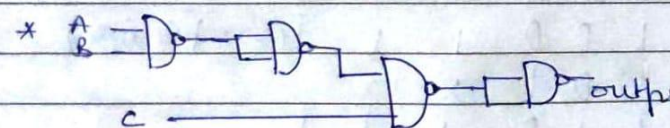*  output [using 3-input NAND Gate]

*  output [2-input NAND Gate]

Q3.

Ans-3

$D_1 D_0$

00 \rightarrow forward

01 \rightarrow right

10 \rightarrow left

11 \rightarrow reverse

$S_1 S_0$

00 \rightarrow zero

01 \rightarrow low

10 \rightarrow medium

11 \rightarrow high

constraints \rightarrow

high speed \rightarrow for full movement only

rev. dir \rightarrow at low speed only

D_1	D_0	S_1	S_0	P
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

$$\Rightarrow P = f(D_1, D_0, S_1, S_0) = \Sigma(7, 11, 14, 15)$$

$D_1 D_0 \backslash S_1 S_0$	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	1	1	1	1
10	1	1	1	1

$$\Rightarrow P = D_1 D_0 S_1 + D_0 S_1 S_0 + D_1 S_1 S_0$$

$$\Rightarrow P = D_1 D_0 S_1 + S_1 S_0 (D_0 + D_1)$$

Q4.

Ans-4

Temperature & Pressure controlled by Heater (H) & inlet valve (V)

in such a way →

$H=1$; T low & P not high
(heater on)

$V=1$; P low & T not low
(valve open)

$A=1$ when T & P either both low or both high
alarm

Temperature

TL	TH	y
0	0	Normal
0	1	high
1	0	low
1	1	Normal

Pressure

PL	PH	y
0	0	Normal
0	1	high
1	0	low
1	1	Normal

TL	TH	PL	PH	H	V	A
0	0	0	0			
0	0	0	1			
0	0	1	0		1	
0	0	1	1			
0	1	0	0			
0	1	0	1			1
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			
1	1	1	1			

$$H = \sum (8, 10, 11)$$

$$V = \sum (2, 10, 14)$$

$$A = \sum (5, 10)$$

calculation for H

TL TH	PL PH
00	0 1 3 2
01	1 5 7 6
11	14 13 15 12
10	4 9 11 10

$$H = \overline{LTH}(\overline{PH} + PH)$$

calculation for V

TL TH	PL PH
00	0 1 3 2
01	1 5 7 6
11	14 13 15 12
10	4 9 11 10

$$V = \overline{PLPH}(\overline{TH} + TL)$$

calculation for A

TL TH	PL PH
00	0 1 3 2
01	1 5 7 6
11	14 13 15 12
10	4 9 11 10

$$A = \overline{TLTH} \overline{PLPH} + \overline{TLTH} PLPH$$

Q5.

Solⁿ:

$x_1, x_2, x_3 \Rightarrow 3 \text{ keys}$

Let output be "Y" (logic high when two or more keys are used).

Truth Table

x_1	x_2	x_3	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1 ✓
1	0	0	0
1	0	1	1 ✓
1	1	0	1 ✓
1	1	1	1 ✓

$$\{x + \bar{x} = 1\}; \{x + \bar{x}y = x + y\}$$

$$Y = \bar{x}_1 \cdot x_2 \cdot x_3 + x_1 \cdot \bar{x}_2 \cdot x_3 + x_1 \cdot x_2 \cdot \bar{x}_3 + x_1 \cdot x_2 \cdot x_3$$

$$= \bar{x}_1 \cdot x_2 \cdot x_3 + x_1 \cdot \bar{x}_2 \cdot x_3 + x_1 \cdot x_2 (\bar{x}_3 + x_3)$$

$$= \bar{x}_1 \cdot x_2 \cdot x_3 + x_1 \cdot \bar{x}_2 \cdot x_3 + x_1 \cdot x_2$$

$$= \bar{x}_1 \cdot x_2 \cdot x_3 + x_1 (\bar{x}_2 \cdot x_3 + x_2)$$

$$= \bar{x}_1 \cdot x_2 \cdot x_3 + x_1 (x_2 + x_3)$$


$$= \bar{x}_1 \cdot x_2 \cdot x_3 + x_1 \cdot x_2 + x_1 \cdot x_3$$

$$= x_2 (\bar{x}_1 \cdot x_3 + x_1) + x_1 \cdot x_3$$

$$= x_2 (x_3 + x_1) + x_1 \cdot x_3$$

$$Y = x_1 x_2 + x_2 x_3 + x_3 x_1$$

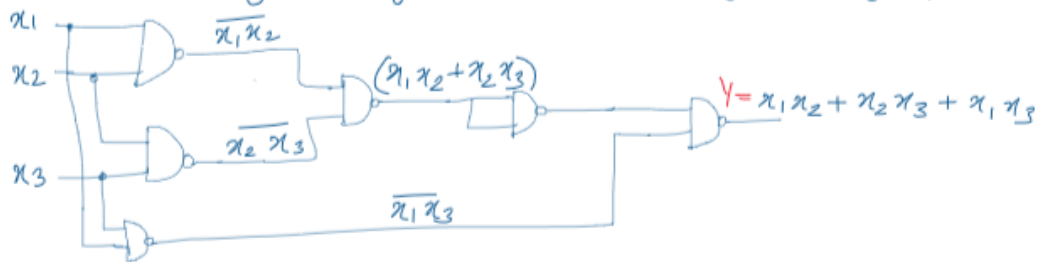Implementing Y using minimum number of NAND gates,



Q6.

Solⁿ: (a) $F_1(A, B, C, D) = \bar{A}B + A\bar{B} + \bar{C}D$

CSOP form,

$$= \bar{A}B(C+Z)(D+\bar{D}) + A\bar{B}(C+\bar{C})(D+\bar{D}) + (A+\bar{A})(B+\bar{B})\bar{C}D$$

$$= \bar{A}B(CD + C\bar{D} + \bar{C}D + \bar{C}\bar{D}) + A\bar{B}(CD + C\bar{D} + \bar{C}D + \bar{C}\bar{D})$$

$$+ (AB + A\bar{B} + \bar{A}B + \bar{A}\bar{B})\bar{C}D$$

$$= \bar{A}BCD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + A\bar{B}CD + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D}$$

$$+ AB\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + AB\bar{C}D + A\bar{B}\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D}$$

$$F_1 = \bar{A}BCD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + A\bar{B}CD + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D}$$

→ CSOP form

(b) $F_1(A, B, C, D) = \bar{A}B + A\bar{B} + \bar{C}D$

This is the minimized SOP form.

Converting SOP to POS (Dual form), $\left\{ \begin{array}{l} \text{AND} \leftrightarrow \text{OR} \\ \text{OR} \leftrightarrow \text{AND} \end{array} \right\}$

$$F_1 = (\bar{A}+B) \cdot (A+\bar{B}) \cdot (\bar{C}+D)$$

→ Minimized POS form.

(c) $F_2(A, B, C, D) = (A+B) \cdot (\bar{C}+\bar{D}) \cdot (C+D)$

$$(c) F_2(A, B, C, D) = (A+B) \cdot (\bar{C} + \bar{D}) \cdot (C+D)$$

① CSOP form

Converting Pos form to SOP form using Dual form.

$$F_2 = A \cdot B + \bar{C} \bar{D} + CD$$

$$F_2 = A \cdot B (C+C)(D+D) + (A+\bar{A})(B+\bar{B}) \bar{C} \bar{D} + (A+\bar{A})(B+\bar{B}) CD$$

$$= AB(CD + C\bar{D} + \bar{C}D + \bar{C}\bar{D}) + (\bar{A}B + A\bar{B} + \bar{A}\bar{B} + A\bar{B}) \bar{C} \bar{D} + (\bar{A}B + A\bar{B} + \bar{A}\bar{B} + A\bar{B}) CD$$

$$= \begin{matrix} \text{1111} & \text{1110} & \text{1101} & \text{1100} & \text{1000} & \text{0100} & \text{0000} \\ ABCD + & ABC\bar{D} + & AB\bar{C}D + & AB\bar{C}\bar{D} + & A\bar{B}\bar{C}\bar{D} + & \bar{A}\bar{B}\bar{C}\bar{D} + & \bar{A}\bar{B}\bar{C}\bar{D} \\ + & \text{1111} & \text{0111} & \text{1011} & \text{0011} & & \\ & ABCD + & \bar{A}BCD + & A\bar{B}CD + & \bar{A}\bar{B}CD & & \end{matrix}$$

$$F_2 = ABCD + ABC\bar{D} + AB\bar{C}D + AB\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}BCD + A\bar{B}CD + \bar{A}\bar{B}CD$$

→ CSOP form

② Minimized Pos form

$$F_2 = (A+B) \cdot (\bar{C} + \bar{D}) \cdot (C+D)$$

↳ The expression is in minimized Pos only.

Q7.

Using postulates,

a. find minimum SOP expression for the function,

$$F(A, B, C) = A \cdot C + A \cdot B' + A' \cdot B \cdot C + A' \cdot B' \cdot C'$$

b. Prove that $B \oplus (A \cdot B + B \cdot C + A' \cdot C) = A' \cdot (B \oplus C)$

$$\begin{aligned}
 \underline{\text{Sol}}^M: (a) \quad F(A, B, C) &= AC + A\bar{B} + \bar{A}BC + \bar{A}\bar{B}\bar{C} \\
 &= C(A + \bar{A}B) + \bar{B}(A + \bar{A}\bar{C}) \\
 &= C(A + B) + \bar{B}(A + \bar{C}) \\
 &= AC + BC + A\bar{B} + \bar{B}\bar{C}
 \end{aligned}$$

$$\left\{ \begin{array}{l} \therefore, \quad XY + YZ + \bar{X}Z = XY + \bar{X}Z \\ \quad \quad X + \bar{X}Y = X + Y \end{array} \right\} \Rightarrow \text{Postulate}$$

$$F(A, B, C) = BC + A\bar{B} + \bar{B}\bar{C}$$

$$(b) \quad B \oplus (A \cdot B + B \cdot C + \bar{A} \cdot C) = \bar{A} \cdot (B \oplus C)$$

$$\left\{ \therefore AB + BC + \bar{A}C = AB + \bar{A}C \Rightarrow \text{Postulate} \right\}$$

$$\underline{\text{LHS}}: \Rightarrow B \oplus (AB + \bar{A}C)$$

$$= \bar{B} \cdot (AB + \bar{A}C) + B \cdot (\overline{AB + \bar{A}C})$$

$$= AB \cdot \bar{B} + \bar{A}\bar{B}C + B(\overline{A \cdot B} \cdot \overline{\bar{A}C})$$

$$\left\{ \begin{array}{l} \therefore, \quad X \cdot \bar{X} = 0 \\ \quad \quad \overline{X \cdot Y} = \bar{X} + \bar{Y} \\ \quad \quad \overline{X + Y} = \bar{X} \cdot \bar{Y} \end{array} \right\}$$

$$= 0 + \bar{A}\bar{B}C + B \cdot [(\bar{A} + \bar{B}) \cdot (A + \bar{C})]$$

$$= \bar{A}\bar{B}C + B[\cancel{\bar{A}}\overset{0}{A} + \bar{A}\bar{C} + A\bar{B} + \bar{B}\bar{C}]$$

$$= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \cancel{AB\bar{B}}^0 + \cancel{B \cdot \bar{B}\bar{C}}^0$$

$$= \bar{A}(\bar{B}C + \bar{B}\bar{C})$$

$$= \bar{A}(B \oplus C) \Rightarrow \text{R.H.S}$$

Hence Proved

Q8.

Sol: (a)

Input			Outputs	
A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

for S,

$$(CSOP): S = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$(CPOS): S = (A+B+C_{in}) \cdot (A+\bar{B}+\bar{C}_{in}) \cdot (\bar{A}+B+\bar{C}_{in}) \cdot (\bar{A}+\bar{B}+C_{in})$$

Minimized SOP form,

$$S = \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in}$$

$$= C_{in}(\bar{A}\bar{B} + AB) + \bar{C}_{in}(\bar{A}B + A\bar{B})$$

$$= C_{in}(\overline{A \oplus B}) + \bar{C}_{in}(A \oplus B)$$

$$= (A \oplus B) \oplus C_{in}$$

$$= \underline{A \oplus B} \oplus C_{in}$$

$$\{ \text{Let } A \oplus B = P \}$$

$$= P \oplus C_{in}$$

$$= P\bar{C}_{in} + \bar{P}C_{in}$$

$$= (P + C_{in})(\bar{P} + \bar{C}_{in})$$


$$\{ \text{Let } \bar{P} + \bar{C}_{in} = Q \} \Rightarrow \text{for simplicity}$$

$$= Q(P + C_{in})$$


$$= \bar{Q}P + Q\bar{C}_{in}$$

$$S = \overline{\bar{Q} \cdot P \cdot Q \cdot C_{in}}$$
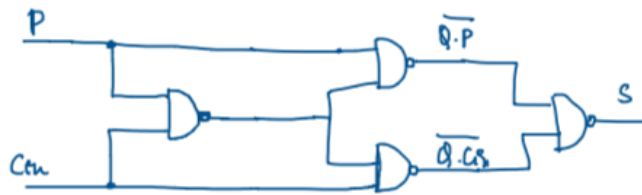
$$\left\{ \begin{matrix} P \\ C_{in} \end{matrix} = D-Q \right\}$$



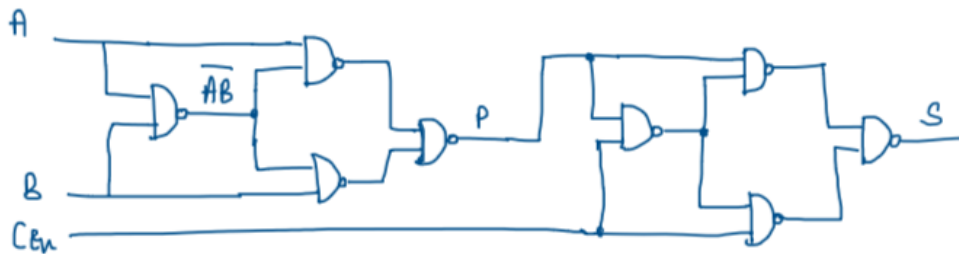Now, $P = A \oplus B$ so we can repeat the above steps for A & B.



for Cout,

$$\text{CSOP: } C_{out} = \bar{A}B C_{in} + A\bar{B} C_{in} + AB\bar{C}_{in} + ABC_{in}$$

$$\text{CPOS: } C_{out} = (A+B+C_{in}).(A+B+\bar{C}_{in}).(A+\bar{B}+C_{in}).(\bar{A}+B+C_{in})$$

Minimizing in SOP form,

$$\Rightarrow \bar{A}B C_{in} + A\bar{B} C_{in} + AB\bar{C}_{in} + ABC_{in}$$

$$\Rightarrow \bar{A}B C_{in} + A\bar{B} C_{in} + AB(\bar{C}_{in} + C_{in})$$

$$\Rightarrow \bar{A}B C_{in} + A\bar{B} C_{in} + AB(1)$$

$$\Rightarrow \bar{A}B C_{in} + A(B + \bar{B} C_{in})$$

$$\Rightarrow \bar{A}B C_{in} + A(B + C_{in})$$


$$\Rightarrow \bar{A}B C_{in} + AB + AC_{in}$$

$$\Rightarrow C_{in}(\bar{A}B + A) + AB$$

$$\Rightarrow C_{in}(A+B) + AB$$

$$\boxed{C_{out} \Rightarrow AB + BC_{in} + C_{in}A}$$
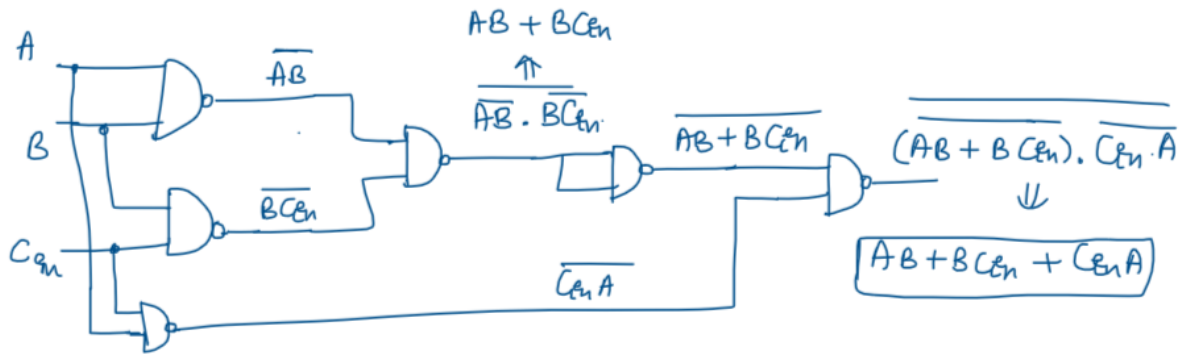
$$\left. \begin{array}{l} \Rightarrow \bar{A}B C_{in} + A(B + \bar{B} C_{in}) \\ \Rightarrow \bar{A}B C_{in} + A(B + C_{in}) \end{array} \right\} \because X + \bar{X}Y = X + Y$$



(b)

Inputs				Output
A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

CSOP


$$F = \overline{A}\overline{B}CD + \overline{A}B\overline{C}D + A\overline{B}CD + AB\overline{C}\overline{D} + AB\overline{C}D + ABC\overline{D} + ABCD$$

CPOS

$$F = (A+B+C+D) \cdot (A+B+C+\overline{D}) \cdot (A+B+\overline{C}+D) \cdot (A+B+\overline{C}+\overline{D}) \cdot (A+\overline{B}+C+D) \cdot (\overline{A}+B+C+D) \cdot (\overline{A}+\overline{B}+C+D)$$

Minimizing,

$$\begin{aligned}
 F &= \overline{A}\overline{B}CD + \overline{A}B\overline{C}D + A\overline{B}CD + AB\overline{C}\overline{D} + AB\overline{C}D + ABC\overline{D} + ABCD \\
 &= \overline{B}CD(\overline{A}+A) + B\overline{C}D(\overline{A}+A) + AB\overline{C}(\overline{D}+D) + ABC\overline{D} \\
 &= \overline{B}CD + B\overline{C}D + AB\overline{C} + ABC\overline{D} \\
 &= CD(\overline{B}+B) + AB\overline{C} + ABC\overline{D} \quad \left\{ \begin{array}{l} x + \overline{x}y = x + y \\ x + \overline{x} = 1 \end{array} \right\} \\
 &= CD + AB\overline{C} + ABC\overline{D} \\
 &= AB\overline{C} + C(D + AB\overline{D}) \\
 &= AB\overline{C} + C(D + AB) \\
 &= AB\overline{C} + CD + ABC \\
 &= AB(\overline{C} + C) + CD \\
 &\boxed{F = AB + CD}
 \end{aligned}$$

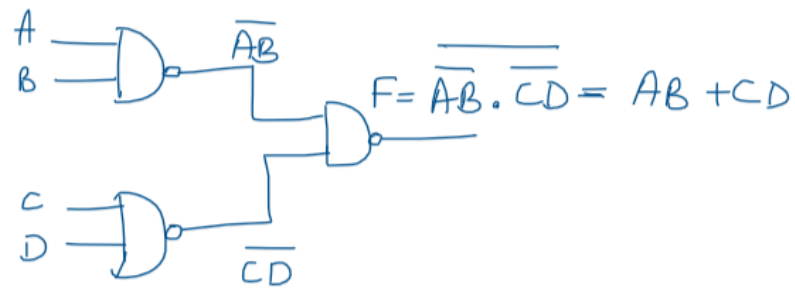

Q9. Prove that $A'B(D' + C'D) + B(A + A'CD) = B$

Solⁿ: $\bar{A}B(\bar{D} + \bar{C}D) + B(A + \bar{A}CD) = B$

LHS: $\bar{A}B(\bar{D} + \bar{C}D) + B(A + \bar{A}CD)$

$\left\{ \text{using } x + \bar{x}y = x + y \right\}$

$$= \bar{A}B(\bar{D} + \bar{C}) + B(A + CD)$$

$$= \bar{A}B\bar{D} + \bar{A}B\bar{C} + AB + BCD$$

$$= B[\bar{A}\bar{D} + (\bar{A}\bar{C} + A) + CD]$$

$$= B[\bar{A}\bar{D} + \bar{C} + A + CD]$$

$$= B[(\bar{A}\bar{D} + A) + (\bar{C} + CD)]$$

$$= B[\bar{D} + A + \bar{C} + D]$$


$$= B[1 + A + \bar{C}]$$

$$= B[1]$$

$$= B \Rightarrow \underline{\text{R.H.S}} \checkmark$$

$\left\{ \text{using } x + \bar{x} = 1 \right\}$

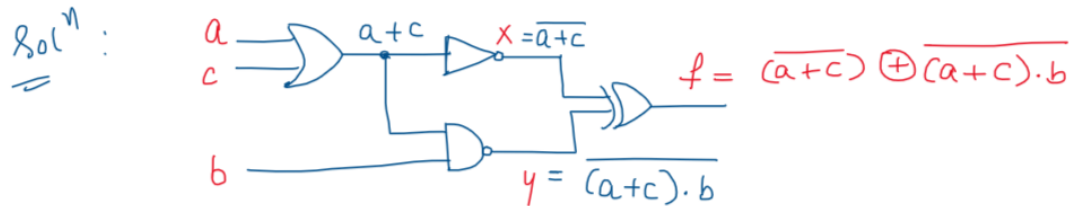Q10. Assuming zero delay between input and output of each gate, complete the timing diagram of the following circuit. (In answer sheet, show all 6 timing diagrams corresponding to boolean variables a,b,c,x,y,f on the same page).



Truth-Table

a	b	c	x $\overline{a+c}$	y $(a+c).b$	f $x \oplus y$
0	0	0	1	1	0
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	0	1	1
1	0	1	0	1	1
1	1	0	0	0	0
1	1	1	0	0	0

